

# Contents

<b>1</b>	<b>Objectives</b>	<b>2</b>
<b>2</b>	<b>Tools Used</b>	<b>2</b>
<b>3</b>	<b>Schematics and Outputs</b>	<b>2</b>
<b>4</b>	<b>Results</b>	<b>7</b>
<b>5</b>	<b>Observations</b>	<b>7</b>
<b>6</b>	<b>Conclusions</b>	<b>8</b>

# 1 Objectives

- Analysis and design of CMOS transconductance amplifier.
- Find maximum output swing ,maximum gain,maximum possible band-width maximum power with suitable aspect ratio.

# 2 Tools Used

- LTspice IV

# 3 Schematics and Outputs

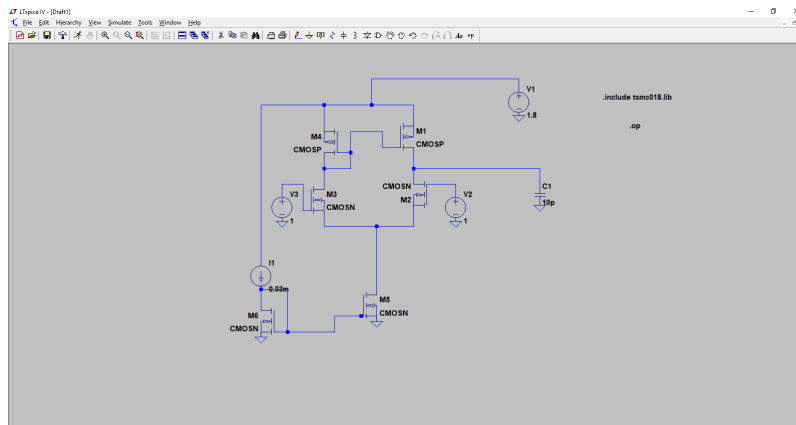


Figure 1: Schematic for operating currents

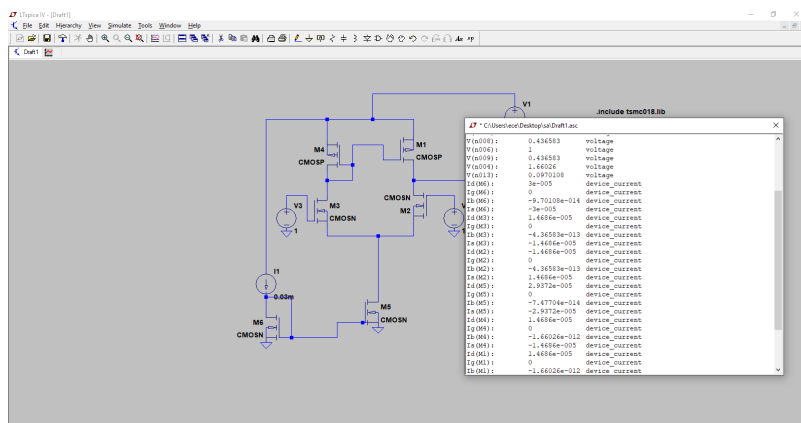


Figure 2: Operating currents

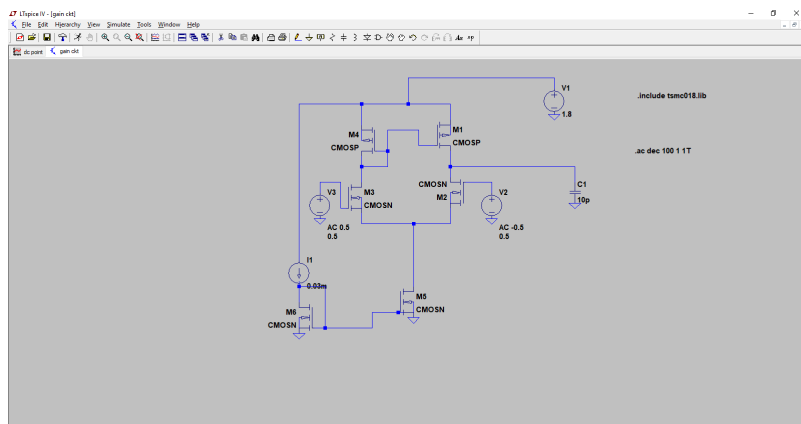


Figure 3: Gain schematic

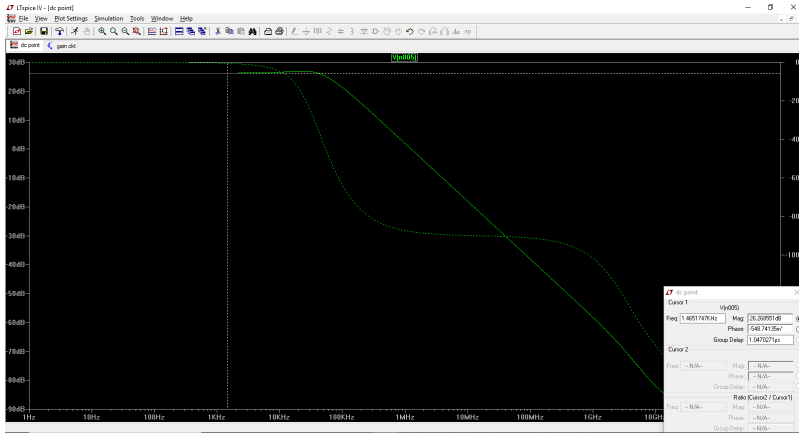


Figure 4: Gain

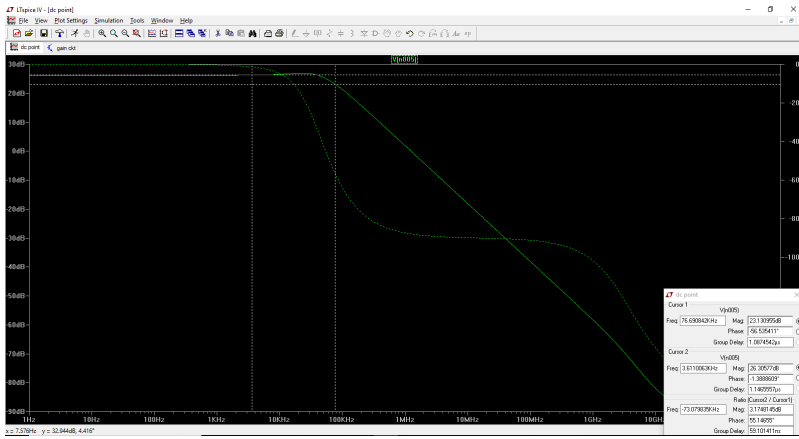


Figure 5: 3 db cutoff

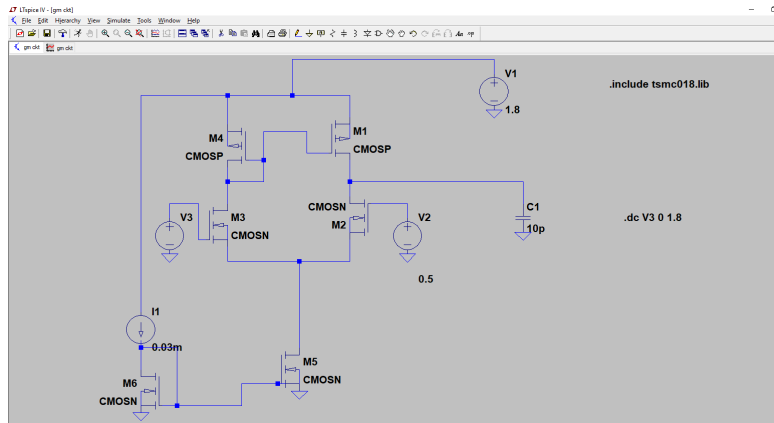


Figure 6: schematic for transconductance

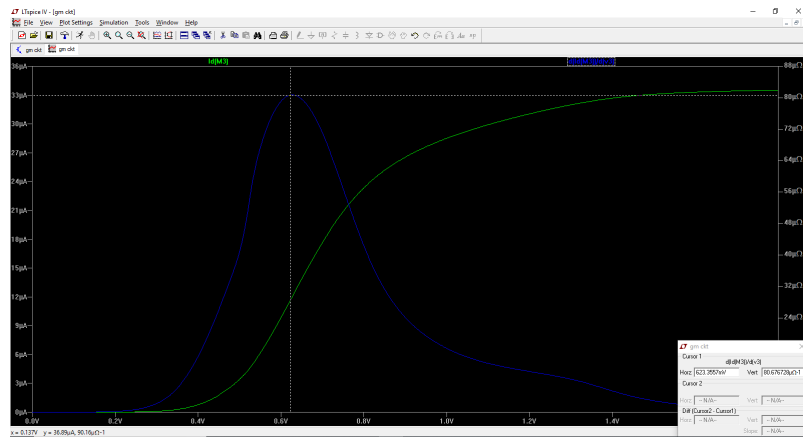


Figure 7: transconductance

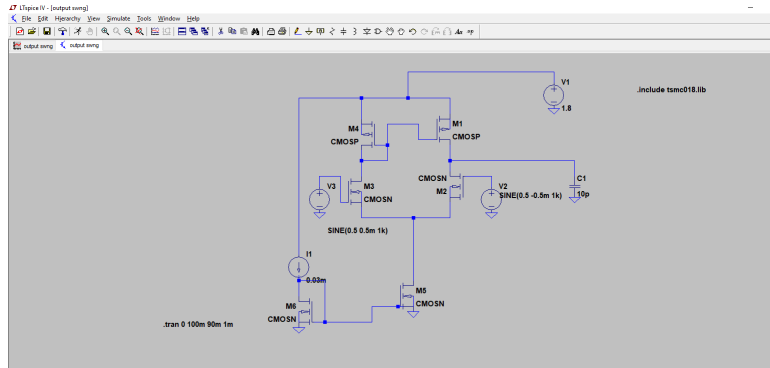


Figure 8: schematic for output swing

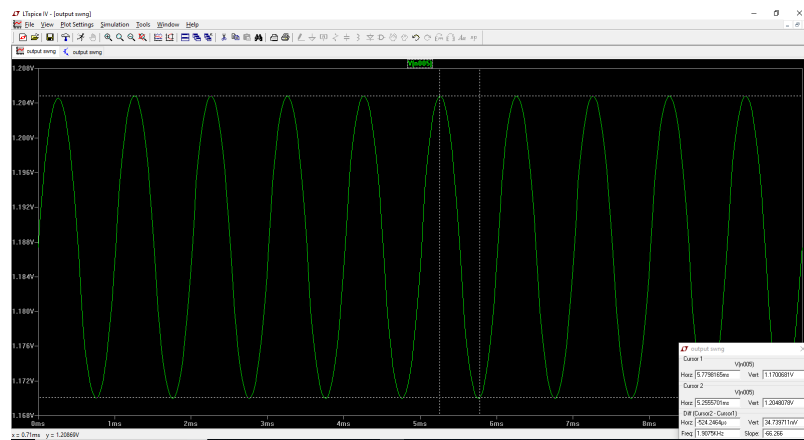


Figure 9: output swing

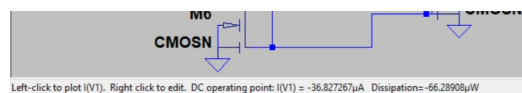


Figure 10: power consumption

## 4 Results

- AC Gain = 26.26 dB
- 3 db Bandwidth= 76.69 KHz
- output swing=34.73 mV
- power consumption= 66.28  $\mu$  W
- transconductance  $g_m$ = 80.67  $\mu\Omega^{-1}$

## 5 Observations

- The source voltage = 1.8 V.
- Load capacitance = 10 pF
- $\frac{W}{L}$  RATIOS

$(W : L)_{M1}$	$\frac{360n}{180n}$
$(W : L)_{M2}$	$\frac{720n}{180n}$
$(W : L)_{M3}$	$\frac{720n}{180n}$
$(W : L)_{M4}$	$\frac{360n}{180n}$
$(W : L)_{M5}$	$\frac{450n}{180n}$
$(W : L)_{M6}$	$\frac{360n}{180n}$

- PMOS current mirror is used to provide bias current to NMOS differential input and single ended amplifier.
- The W/L ratios were selected such that M1 and M4 carry equal currents.
- NMOS current mirror was used to provide tail current.
- By changing the  $\frac{W}{L}$  ratios of transistors M2 and M3 the gain of the circuit changes.
- By increasing  $\frac{W}{L}$  ratios of M2 and M3 the gain increases.

## 6 Conclusions

- Operational transconductance amplifier is a Voltage controlled current source.
- Operational transconductance amplifier is a differential input and single ended output amplifier.
- OTA rejects input noise.
- The circuit has a pole at frequency  $\frac{1}{2\pi R_{out}C}$  where slope of the gain falls by 20dB per decade.
- It has high  $R_{out}(r_{o1}||r_{o2})$ .
- The gain bandwidth product of the circuit is constant.